

CHAPTER 6


Single-Stage Integrated-Circuit Amplifiers

Frequency Response

- **Zeros and poles: dominant pole (at least two octaves away from the nearest pole or zero)**
- **Open circuits time constants**
- **Miller's theorem**

6.6 High-Frequency Response of The CS and CE Amplifiers

6.6.5 The situation when R_{sig} is low


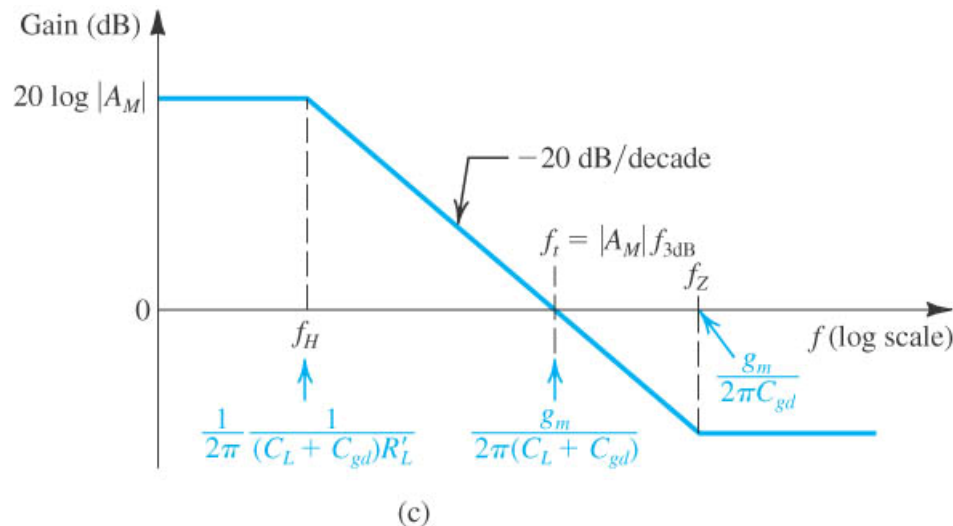


Gain-bandwidth product

$$f_t = |A_M| f_H = g_m R'_L \frac{1}{2\pi(C_L + C_{gd})R'_L} = \frac{g_m}{2\pi(C_L + C_{gd})}$$


6.7 The CG and CB Amplifier With Active Load

6.7.1 The Common Gate Amplifier

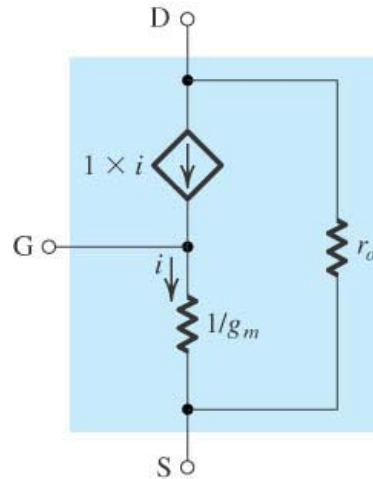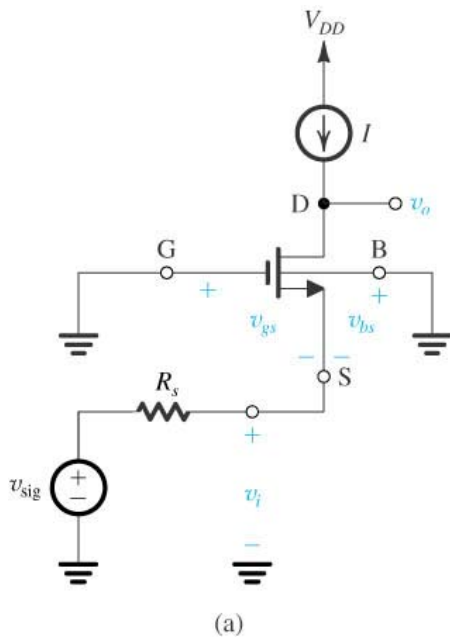

Drain Current:

$$g_m v_{gs}$$

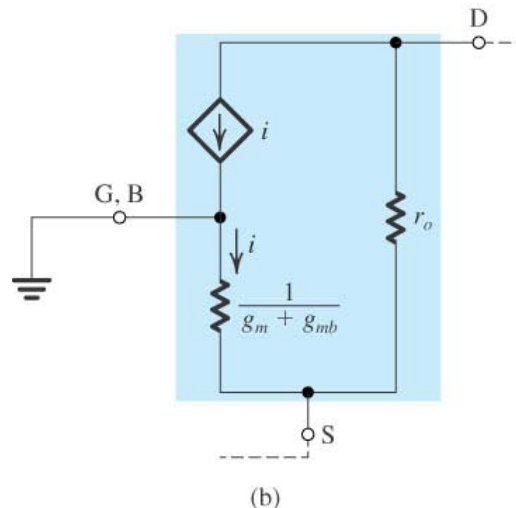

The Body Effect

$$g_m v_{gs} + g_{mb} v_{bs}$$



$$g_{mb} = \chi g_m \quad \chi = 0.1 \sim 0.2$$

for $v_{gs} = v_{bs}$

$$(g_m + g_{mb}) v_{gs}$$

6.7 The CG and CB Amplifier With Active Load

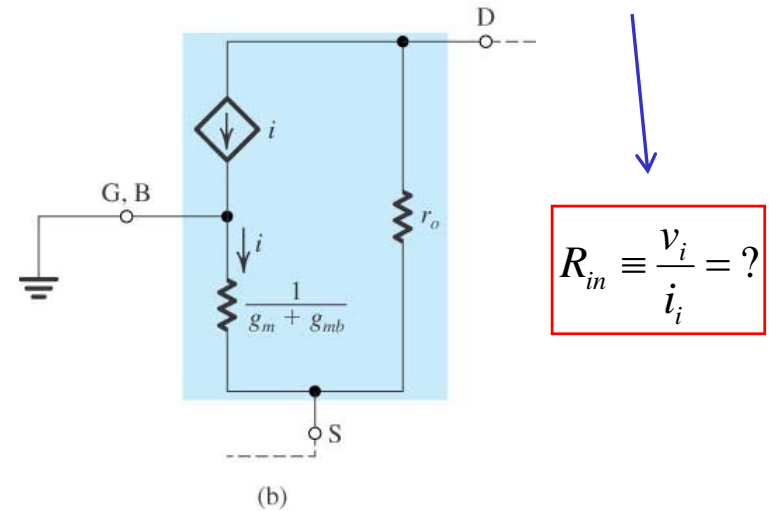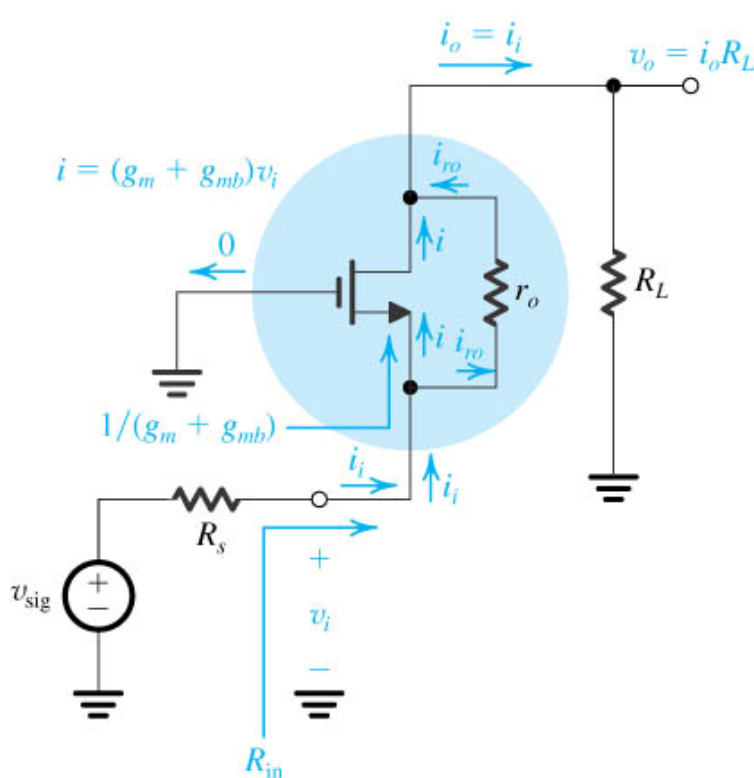6.7.1 The Common Gate Amplifier: *Input Resistance*



$$R_{in} \equiv \frac{v_i}{i_i} = ?$$



$$R_{in} \equiv \frac{v_i}{i_i} = \frac{r_o + R_L}{1 + (g_m + g_{mb})r_o} \quad r_o \rightarrow \infty ?$$

$$(c) \begin{cases} i_i = (g_m + g_{mb})v_i + i_{ro} \\ i_{ro} = \frac{v_i - v_o}{r_o} = \frac{v_i - i_i R_L}{r_o} \end{cases} \Rightarrow$$

$$i_i = \left(g_m + g_{mb} + \frac{1}{r_o} \right) v_i / \left(1 + \frac{R_L}{r_o} \right)$$

6.7 The CG and CB Amplifier With Active Load

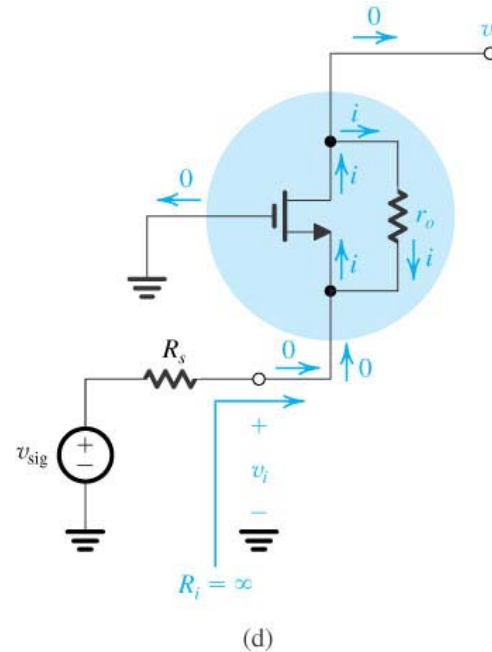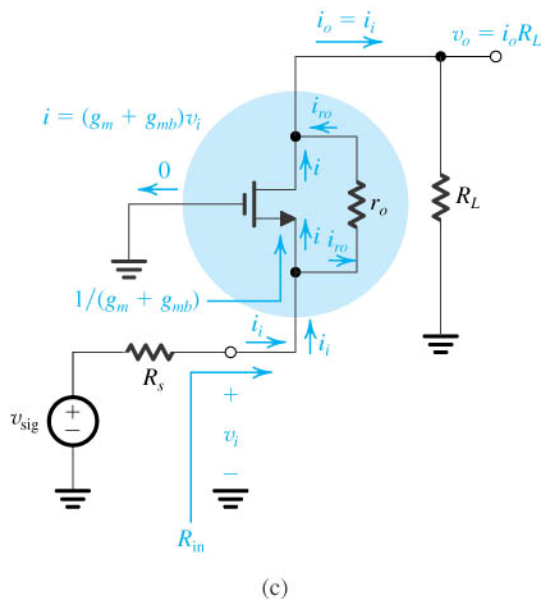6.7.1 The Common Gate Amplifier: $R_L \rightarrow \infty$



$$R_i \equiv \left. \frac{v_i}{i_i} \right|_{R_L = \infty} = ?$$

$$R_{in} \equiv \frac{v_i}{i_i} = \frac{r_o + R_L}{1 + (g_m + g_{mb})r_o}$$

$$R_i = \frac{v_i}{i_i} = \infty$$


$$v_o = i r_o + v_i = (g_m + g_{mb})r_o v_i + v_i$$

$$\frac{v_o}{v_i} = 1 + (g_m + g_{mb})r_o > 0 \quad \text{noninverting}$$

6.7 The CG and CB Amplifier With Active Load

6.7.1 The Common Gate Amplifier:

Output Resistance R_o : $v_i = 0$

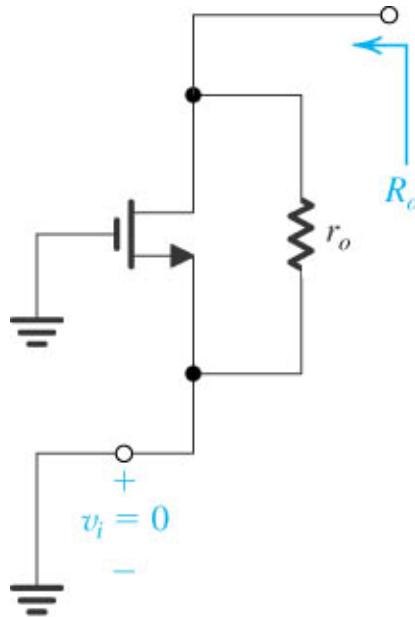


(a)

$$R_o \equiv \left. \frac{v_x}{i_x} \right|_{v_i=0} = r_o$$

6.7 The CG and CB Amplifier With Active Load

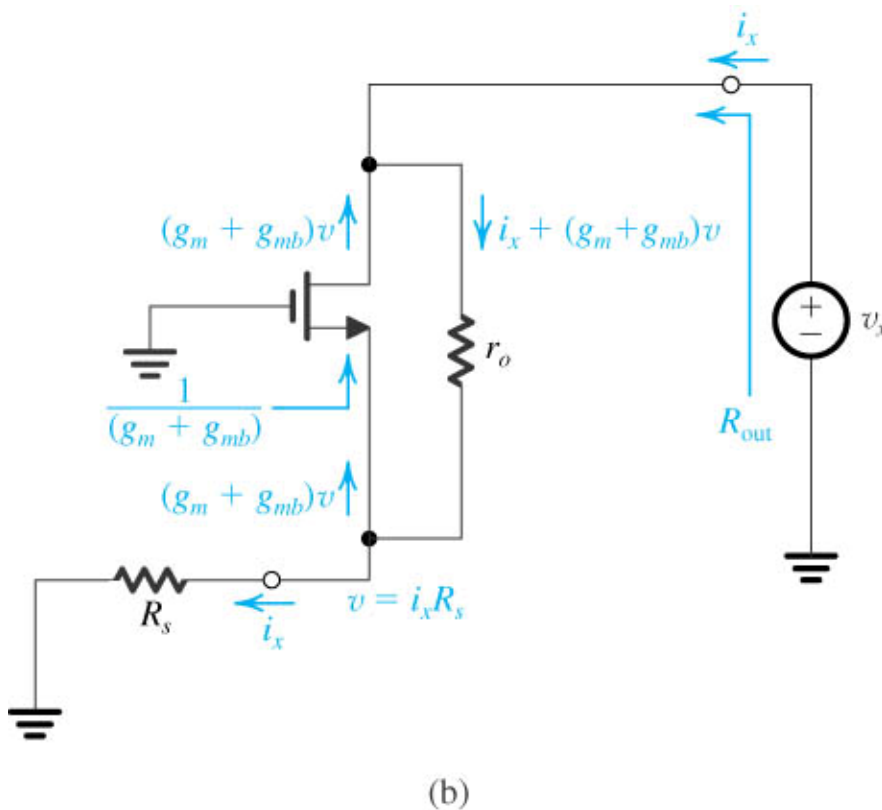6.7.1 The Common Gate Amplifier:


Output Resistance R_{out} : $v_{sig} = 0$



$$\begin{cases} v = i_x R_s \\ v_x = [i_x + (g_m + g_{mb})v]r_o + v \end{cases}$$
$$R_{out} \equiv \frac{v_x}{i_x} = r_o + [1 + (g_m + g_{mb})r_o]R_s$$


6.7 The CG and CB Amplifier With Active Load

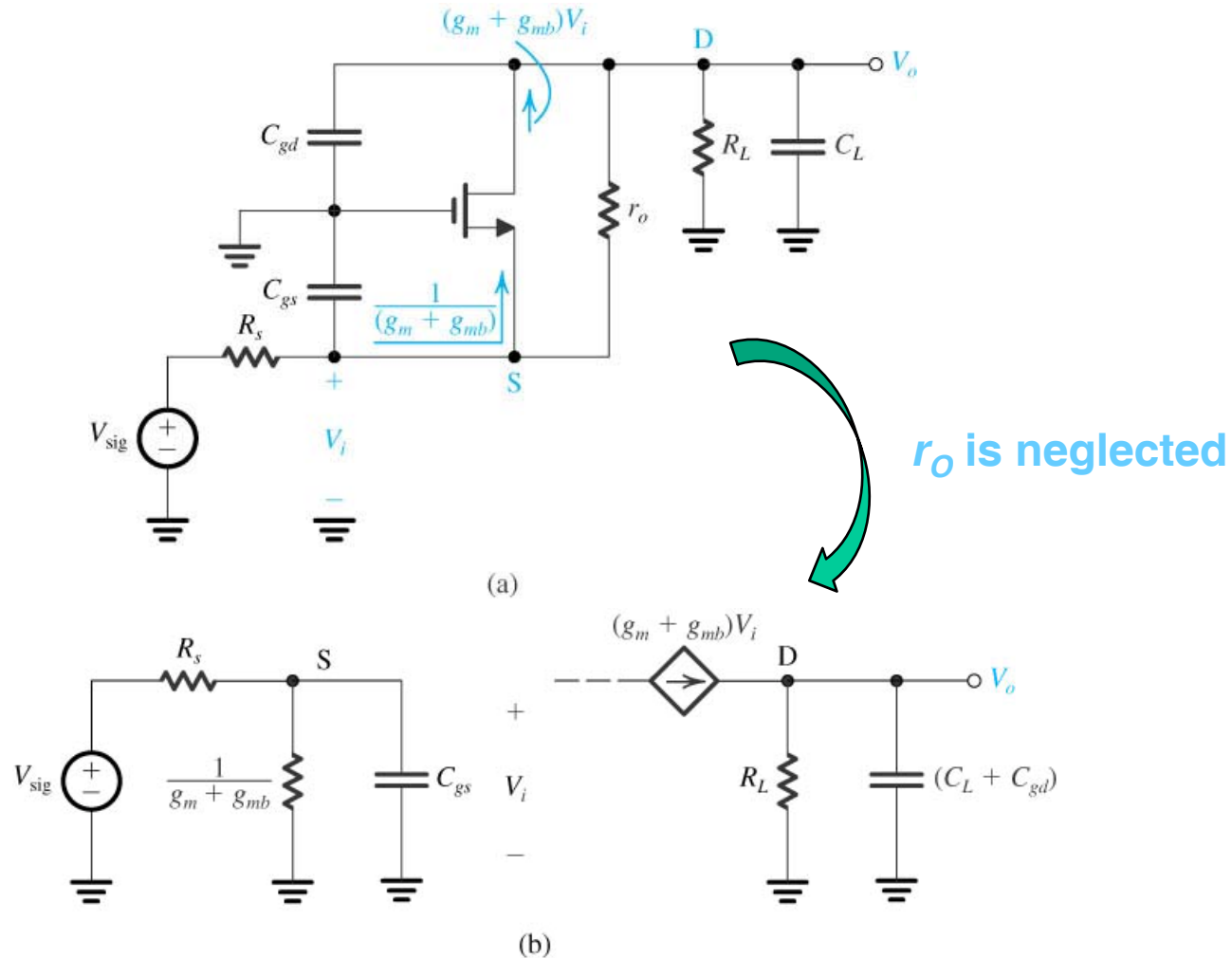6.7.1 The Common Gate Amplifier: *High-frequency*



6.7 The CG and CB Amplifier With Active Load

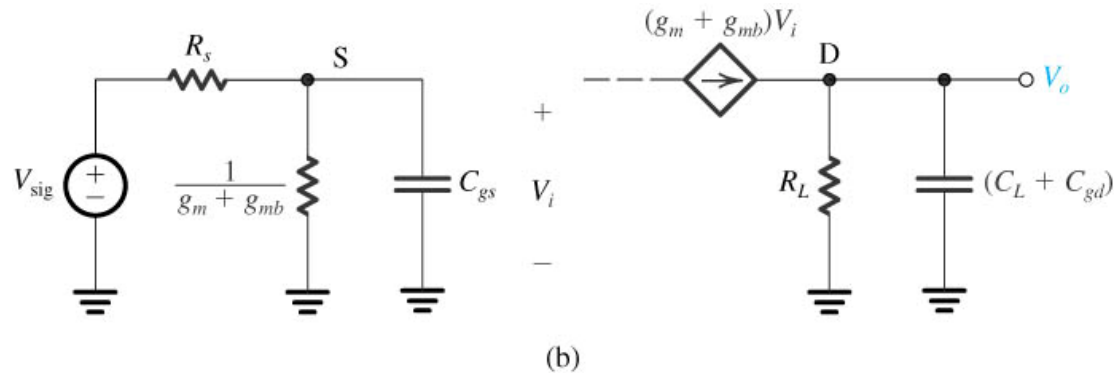6.7.1 The Common Gate Amplifier: *High-frequency*



Two poles (r_o is neglected):

$$f_{P1} = \frac{1}{2\pi C_{gs} \left(R_s \parallel \frac{1}{g_m + g_{mb}} \right)}$$

$$f_{P2} = \frac{1}{2\pi (C_{gd} + C_L) R_L}$$

f_{p1} and f_{p2} are usually higher than the frequency of the dominant input pole in the CS stage

Homework

6.67, 6.74, 6.79, D6.83, 6.86

Project